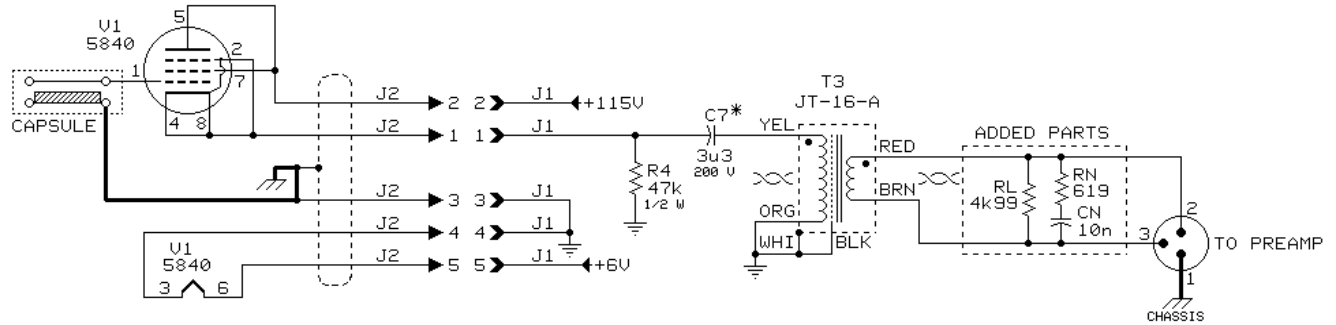


USING THE JT-16-A WITH "THE COUNTRY BOY'S CAPACITOR MICROPHONE"

Article by David Royer in Glass Audio (vol 8, no 1, 1996)



NOTES

SINCE THIS APPLICATION USES THE JT-16-A "BACKWARDS", ITS LOAD RESISTOR AND RC DAMPING NETWORK ARE INTENTIONALLY DIFFERENT FROM THE DATA SHEET. VALUES SHOWN HERE OPTIMIZE HIGH FREQUENCY TRANSIENT RESPONSE AND EXTEND AND FLATTEN LOW FREQUENCY RESPONSE.

*THE ORIGINAL VALUE FOR C7 PRODUCES A LOW FREQUENCY RESPONSE 3 dB DOWN AT 10 Hz. LARGER VALUES WILL EXTEND LF RESPONSE PROPORTIONALLY.

ALL RESISTORS ARE ±1% 1/4w METAL FILM TYPES, ROEDERSTEIN MK2-1 OR EQUIVALENT (unless noted otherwise)

ALL RESISTORS IN OHMS (4k99 = 4.99k, 30r1 = 30.1)

ALL CAPACITORS IN FARADS (10n = .01u = 10,000p)

USE OF GOLD PLATED CONTACTS IN XLR CONNECTORS IS HIGHLY RECOMMENDED

TIGHTLY TWIST PAIRS OF LEADS SHOWN AS ><><

KEEP ALL WIRING AS SHORT AS POSSIBLE

jensen	AS076
	03/13/96
7135 HAYVENHURST AVE. VAN NUYS, CALIFORNIA 91406 (213) 876-0059	

© COPYRIGHT 1996, JENSEN TRANSFORMERS, INC.